

ELEC-H-409

Th05: Analysis of circuit performance:  
timing, power and area

Dragomir Milojevic  
Université libre de Bruxelles

# Today

1. Delays in logic circuits
2. Practical timing analysis and system performance
3. Design for performance
4. Design flow and Performance, Power & Area (PPA) in FPGAs
5. Physical implementation of FPGA circuits


# 1. Delays in logic circuits

# Circuit delays – overview

- Total circuit delay will depend on the delay of its components:
  - A. **Combinatorial delay** – gates, memories, LUTs in FPGAs etc.
  - B. **Sequential delay** – linked to flip-flops (FFs)
  - C. **Wire delay** – due to interconnect (nets)
- Delays are calculated using resistance  $R$ , inductance  $L$  & capacitance  $C$  values of all components – **parasitics**
- **Exact delays** of the circuit will be known only **after placement & route** (P&R) of the design
- This is because during P&R the circuit will undergo different **circuit optimizations** driven by **design constraints**: form of logic circuit & gates could change, but the functionality will of course remain preserved
- If exact parasitics are not known, e.g. wire RLC during synthesis, they can be predicated using more or less complex estimators
 
## A. Combinatorial delays 1/3

- We speak of **timing arcs** – paths from input(s) to output(s) for which we can define a delay; only one timing arc for an inverter:



- Depending on the gate function and input data we speak of **gate rise** or **gate fall** time – time difference between input that reached 50% of it's value and the output reaching the same level
- Gate delay depend on:
  - ▷ **Input transition time (slew)** – time needed to move from 10 to 90% (or 30 to 70% for more recent CMOS) of the maximum value
  - ▷ **Output load** – input pin capacitance of the connected gate


## A. Combinatorial delays 2/3

- Depending on how do we model transition times, we will have more or less accurate delay models:
  - ▶ **Ideal circuits** – no parasitics, no input transition times, zero load, so no rising or falling times  $\rightarrow$  good for theory only
  - ▶ **Linear models** – combine transition time  $TT$  & load  $C_L$ ; better approximation, used in the past for old CMOS technologies:

$$\delta = \delta_0 + \delta_1 TT + \delta_2 C_L$$

where  $\delta_i$  are constants depending on the technology

 - ▶ **Non-Linear Delay Models (NLDM)** – approximated with a number of points stored as 2D matrices: delay is specified as a function of  $TT$  and  $C_L$



## A. Combinatorial delays 3/3



- Once the logic functionality is assembled using transistors devices, electrical simulations are performed to extract different points of the NDLM model that are stored in a **technology library**, example:

```
1 pin (OUT) {  
2     max_transition : 1.0;  
3     timing() {  
4         related_pin : "INP1";  
5         timing_sense : negative_unate;  
6         cell_rise(delay_template_3x3) {  
7             index_1 ("0.1, 0.3, 0.7"); /* Input transition */  
8             index_2 ("0.16, 0.35, 1.43"); /* Output capacitance */  
9             values (  
10                /* 0.16 0.35 1.43 */  
11                /* 0.1 */ "0.0513, 0.1537, 0.5280"  
12                /* 0.3 */ "0.1018, 0.2327, 0.6476",  
13                /* 0.7 */ "0.1334, 1.43*/0.2973, 0.7252"  
14            );  
        }  
    }  
}
```

- During timing analysis SW tool will interpolate between different points – gate transistor model is abstracted (remember Gajski) & simulation process at gate-level is significantly accelerated
- For FPGAs circuits these are stored in (proprietary) **device models**
  
## B. Timing for Flip-Flops (FF) 1/3


- Specification of D-FF:  
*"if control and data input signals change at the same time, it will be the value of the input data just before the control signal change that will be stored"*
- This assumption is important to clarify what will happen in case of simultaneous events on Clk and D (inputs are seen as random)
- In another words input data **must arrive before clock rising edge** of the control signal (i.e. clock) – **set-up time**; data should also be kept stable **sometime after** the clock edge – **hold-time**




 
## B. Timing for Flip-Flops (FF) 2/3


- If set-up and hold times are not respected, **FF will NOT operate correctly** – value stored is not deterministic, i.e. it can't be predicted, could be 0 or 1 (not handy); functional correctness of the memory element is compromised – **metastability problem**
- Any FF will have synchronous outputs ( $Q/Q_n$ ); data on these pins will appear after certain delay with respect to the clock edge – **clock to output**



- Absolute set-up & hold and clock to output time will depend on CMOS device, just like for the INV; they will be characterized upfront and relevant information stored in technology library
 
## B. Timing for Flip-Flops (FF) 3/3

- Typical digital circuits (even combinatorial ones) are implemented as a set of input (source) and output (destination) FFs with gates or LUTs in the cloud in between – this is why we speak of digital systems described as **Register Transfer Logic – RTL**



- On a first rising edge – **clock launch edge** data is captured on D1 & will become available at source FF output after some time
- Data then travels through logic & wires (LUTs) & should arrive before the next **capture** rising edge of the destination FF


## C. Wire delays 1/5

- In the early years we could neglect wire delays: they were too small compared to gate delays
- With CMOS scaling wire delays become more important: today not uncommon to have them contribute for 50% of critical path!
- Delays in wires depend on:
  - ▷ **wire material** – known in advance (Al, Cu, but other materials too)
  - ▷ **wire cross-section** – known in advance for ICs (including FPGAs)
  - ▷ **wire length** – **this is design and place & route dependent**
- It is thus because of this dependency to routing that the actual circuit timing could be known only after routing
- Timing after previous stages of the design flow will use wire delays models approximating the length
  - ▷ After **synthesis** – length predicted based on gate count & gate connectivity
  - ▷ After **placement** – length based on gates, LUTs  $x,y$  positions
  - ▷ After **routing** – real things since real physical nets (wires)
 
## C. Wire delays 2/5

- For a wire of an arbitrary length  $L$ , width  $W$  & height  $H$  capacitance can be calculated using:

$$\begin{aligned} C &= C_{pp} + C_{fringe} \\ &= \frac{\epsilon_{di}}{t_{di}} \mathbf{W}L + \frac{2\epsilon_{di}\pi}{\log(t_{di}/H)} \end{aligned}$$



where  $C_{pp}$  &  $C_{fringe}$  is parallel plate & fringe capacitance,  $t_{di}$  is dielectric thickness and  $\epsilon_{di}$  dielectric constant

- Resistance is computed using:


$$R = \frac{\rho L}{A} = \frac{\rho L}{H\mathbf{W}}$$

where  $\rho$  is resistivity [ $\Omega m$ ]


- Note that  $R$  is inversely &  $C$  directly proportional to  $W$ ; note also that  $RC$  delay is proportional to  $L^2$  (**crucial for any IC**)
 
## C. Wire delay 3/5

- $RC$  delay of a wire is represented using a **distributed RC tree**:



 
- Often simplified  **$\pi$ -lumped** model used instead – total wire capacitance split in half with a total wire resistance in the middle



- Alternative **T-model** splits the resistance value in half, and keeps total wire capacitance  $C_w$  in the middle
 
## C. Wire delay 4/5

- We can then calculate a delay of a source and sink gate connected with a piece of wire of length  $L$  (so  $R_w = rL$  and  $C_w = cL$ )
- Source gate has output resistance  $R_{out}$  driving a  $\pi$ -model of a wire connected to input pin with a cap value of  $C_L$



- Delay of the circuit on the right can be then calculated using **Elmore's delay** approximation (quite rough):


$$D = \frac{1}{2}R_{out}C_w + (R_{out} + R_w)\left(\frac{1}{2}C_w + C_L\right)$$

## C. Wire delay 5/5

- Total  $C$  seen by the driver gate will determine the amount of current drawn; more  $C \rightarrow$  more current is to be delivered
- We have more  $C$ :
  - ▷ If wires are smaller (scaled wires – technology), longer (design)
  - ▷ If we have more input capacitance at sink gate (technology)
  - ▷ If we have Fan-Out (FO)  $> 1$ , i.e. more than one gate connected to the same output (design dependent)
- To deliver necessary current we need to **size gates**; logic functionality is the same but gate internal architecture is more complex – we put more transistors in parallel to increase current delivery capacity; gates have different **drive strengths**
- Higher driver strength gates can deliver more current but for more area & power per gate
- To enable current delivery flexibility FPGAs implement fixed length connections with predictable loads – this comes at a price, reason why FPGAs will be always less optimal than ASICs
 
# Impact of the wire length on delays

- If we scale logic gates, we need to scale wires too; cross section should get smaller but **delay per unit length goes up** – wire will contribute more to critical path; very little can be done here, this is **fundamental problem of CMOS scaling**
- Delay in the wire has **quadratic dependence on  $L$**
- To reduce the impact of  $L$  we break down (long) wire by adding buffers or an even number of inverters – **buffer insertion**
  - ▷ **Why even number of inverters?**




- You will add extra inverter delays, but total delay is now linear function of  $\frac{L}{n}$ , where  $n$  is the number of segments
- This can not go on forever, at one point wire delay is small enough not to justify insertion any more; this can be calculated


 
# Timing at complete circuit level

- For sequential circuits with FFs, with or without feedback, so including combinatorial logic, we can define different **path group** delays that need to be checked once the circuit is completed
  - ▷ **Input port to register** – from the IC pin to the first FF
  - ▷ **Register-to-register** – from clock input of the launching FF and its output, to the capturing FF input and next clock edge
  - ▷ **Register-to-output** – from clock and FF output to output pin



- In FPGAs inputs can be registered at IOB level, (not automated); that way you make sure that input/output delays are minimal
- Because of many IOs and especially many register-to-register paths we need automation to analyze timing at circuit level

## 2. Practical timing analysis and system performance

# Timing Analysis – TA (1/3)

- Place & route process is timing driven, so timing is calculated but locally on a limited parts of the circuit (divide & conquer)
- TA at circuit level is a separated design flow step using dedicated EDA tools (e.g. ModelSim, VCS or similar)
- During TA we derive all individual component delays (gates, wires, FFs) in the design & sum them for **for all paths** in the system; sort them, output worst ones & look at the worst
- TA is one of the most important success criteria of the design flow: we always want the maximum possible performance at lowest price (area & power)
- Two kinds of TA:
  - ▷ **Static Timing Analysis (STA)** – static means **independent of inputs** and assuming worst case; STA is thus pessimistic
  - ▷ **Dynamic Timing Analysis** – logic paths are data dependent; by assuming actual input vectors we can derive the actual logic paths; more accurate analysis at expense of more complex computations

# Timing analysis (2/3)

- STA needs following inputs;
  - ▷ **Design netlist** – it defines logical content & connectivity plus placed & routed design data base which defines geometry aspect of the circuit
  - ▷ **Timing constraints** – target clock(s) period, input / output delays, explicit delays of certain paths, clock assumptions etc. supplied in text files with more or less standardized format
  - ▷ **Technology information** – gate and & wire delays for ASICs, LUTs and wires in FPGAs; information provided by technology manufacturer (CMOS foundry or FPGA vendor)
- During place & routing timing constraints are used to drive the implementation process; this is what we **wish should happen at circuit level**
- During STA same constraints are used to see how close or far **final circuit is from the objective** – difference between what wishes & reality

# Timing analysis (3/3)


- **Worst Negative Slack ( $WNS$ )** – difference between actual arrival time in the critical path & the constraint time (aka worst delay)
  - ▷ If  $WNS < 0$  constraints are too optimistic!
  - ▷ If  $WNS > 0$  by little – timing is met
  - ▷ If  $WNS \gg 0$  we have a margin, you could actually increase the actual  $F$  or re-run everything with more aggressive timing constraints
- **Total Negative Slack ( $TNS$ )** – sum of slacks of all failed paths
  - ▷ Shows constraints relevance at system level; difference between few paths that fail by lot (you may optimize a given block), or many paths that fail by little (constraints are maybe too aggressive)
- To get a realistic idea of timing you may do the following:

$$TP_{i+1} = TP_i - WNS$$

in the next iteration your target period  $TP_{i+1}$  is a corrected value of your previous target period  $TP_i$  with the value of  $WNS$

 
# Maximum frequency

- In FPGA design flows STA is automatically run at each step and **max frequency**  $F_{max}$  is always reported (look at generated txt logs)
- **When you will NOT have the  $F_{max}$  reported?**
- Assume valid data on input pin of the launch FF, so set-up and hold time with respect to rising Clk edge, we can then compute **minimum clock period**  $T_{min}$  for a given circuit
- $T_{min}$  is the sum of delays:
  - ▷ **Clock to output** of first FF (FF1)
  - ▷ **Wire delay** W1 (FF1.Q to INV.I)
  - ▷ **Propagation delay** in the inverter (INV)
  - ▷ **Wire delay** W2 (INV.O to FF2.D)
  - ▷ **Set-up** of second FF (FF2)
- Maximum frequency is then  $F_{max} = \frac{1}{T_{min}}$



 
# Logic complexity (FPGAs)

- Complex combinatorial circuits will be decomposed into multiple LUTs: **this decomposition can be VERY sophisticated** depending on optimization targets (see next section)
- Optimization will trade-off:
  - ▷ **amount of concurrency** – number of functionally independent LUTs that could run in parallel (LUTs 11, 12, 13 below)
  - ▷ **logic depth** – number of LUTs in series (functionally dependent) number of LUTs delays before the output (below 3 LUTs)
- Logic depth is crucial since it defines system critical path(s)


 
# Logic depth and critical path

- Very complex logic functions might result in **logically deep** circuits:




- Logically deep circuits result in huge minimum period, so low operating frequency (bad performance)
- The circuit above is not going to be very fast since there are so many accumulated LUT delays
- Question is how to improve the performance of such circuit; the above situation is going to happen in real circuits
- Modify the computational algorithm, if possible and development time permits ... **or insert a FF** – very common solution


 
# Improving clock speed and system latency

- Long combinatorial paths can be **broken** by inserting a certain number of intermediate FFs to **evenly break the critical path**



- Minimum period  $T_{min}$  will become shorter, so **maximum frequency  $F_{max}$  goes up**; design can run faster
- However the output will be available only after **certain number of cycles – latency**, number of cycles that delay the output from the input (3 in the above example)

# Delay vs. Latency trade-off

- For complex circuits inserting latency on purpose is often mandatory, because the critical paths could be very deep
  - ▷ Think of instruction decoding stage that has to reach all sub-systems in a micro-processor, or complex arithmetic sub-circuits
- We speak of **Flip-Flop insertion**, or **pipelining**; this is the link between the physical design and the system architecture; e.g. in a processor the approach translates into sub-circuits to complete fetch, decode, execute, write operations in pipelined fashion
- **When do we apply pipelining?**
  - ▷ If we have to compute the same thing over many different data! The approach is not good for a single data unit computation
  - ▷ This is because the total computation time per unit does not change; you have better  $F_{max}$ , but more cycles to complete
  - ▷ **By supplying one input data at each clock cycle, we will have one output data at each cycle; this results in higher data throughput and reduction in total execution time**

# Improving design performance at RTL/flow level

- **Design flow tuning** – manipulate different design optimization objectives: chose between performance, area or power as a prime optimization target; easiest thing to do since just a choice of an EDA SW parameter: you change, run sit & wait for result; you only pay run-time (could be significant for bigger designs)
- **Constraints tuning** – tightening (or sometimes relaxing) timing objectives for your design; they drive optimization process during place & route; could be easy or complex depending on the design and your understanding of it
- **RTL rewriting for critical path modules** – tracing down critical paths and enabling local RTL modifications; this can be easy ... or VERY complex
- **Micro-architecture change** – complete system change and re-design; **VERY** complex, done only if really needed

# Improving design performance at device level

- Easiest way to do it: **use more aggressive technology**; better CMOS devices for ASICs/FPGAs at the expense of power & cost
- CMOS process is subject to **local variations** due to IC manufacturing process; circuits from the same wafer may have differences and will be binned according to their performance; faster devices will sell for more; this difference is more significant with advanced CMOS technologies
- So, FPGAs come with different **speed grades** ranging from lower to higher performance (same FPGA device family, and even ICs made on the same wafer)
- Faster FPGA device will have better timing of different components (LUTs, memory devices etc.); you can try this out, but use relatively complex design
- If justified you could pick a faster FPGAs to improve your design performance, but you will have to pay more (that difference may be less than the dev time!)


### 3. Design for performance

# What is in your hands?

- Designers impact is most important (block & system integration)

Micro-architecture definition and quality RTL coding  
are key for a good digital circuit design

- Wrong micro-architecture & bad RTL can never produce a good circuit no matter how good design automation is (10x impact at synthesis and 1.2 at place & route levels)
- Today we speak of **High-Level Synthesis** – from C/C++ to HDLs
- Trust me on this: if you do not know what you are doing, no HLS tool **will be able to generate a great IC**
- In real-world significant efforts will be spend in the back-end implementation, since even few % do make a difference

 

Impact on performance

# Tools and their limits

- While current EDA tools are embedding state of the art knowledge of computer science, algorithms & programming, most of the problems that these SW tools deal with are **very complex** (placement, clock tree synthesis & routing)
- Exact solutions are out of the question & their optimality is always relative; good solutions make a good trade-off between performance, power & area & EDA tool run-time
- To make things worst current CMOS technology (5nm) enable very dense IC designs; these days we see commercial ICs with 60 billion transistors even for general purpose computers
- EDA SW need to deal with huge number of objects (gates, pins etc.) and thus require tremendous CPU power, loads of memory and significant run-times (couple of days are not uncommon)
- Real-world design flow tools come with detailed **design methodologies** – recipes on how to improve design process

# Methodology example for FPGAs and Xilinx

Document below – tons of EDA tool & design related information with RTL coding advices for advanced designs

## UltraFast Design Methodology Guide for the Vivado Design Suite

UG949 (v2015.3) November 23, 2015

### Chapter 2: Using the Vivado Design Suite

|  |    |
|--|----|
| Overview of Using the Vivado Design Suite .....                          | 15 |
| Vivado Design Suite Use Models .....                                     | 19 |
| Configuring IP .....   | 23 |
| Creating IP Subsystems with IP Integrator .....                          | 28 |
| Packaging Custom IP and IP Subsystems .....                              | 32 |
| Creating Custom Peripherals .....  | 33 |
| Logic Simulation .....   | 34 |
| Synthesis, Implementation, and Design Analysis .....                     | 43 |
| Source Management and Revision Control Recommendations .....             | 43 |
| Upgrading Designs and IP to the Latest Vivado Design Suite Release ..... | 60 |

### Chapter 3: Board and Device Planning

|  |     |
|--|-----|
| Overview of Board and Device Planning .....                        | 62  |
| PCB Layout Recommendations .....                                   | 62  |
| Clock Resource Planning and Assignment .....                       | 65  |
| I/O Planning Design Flows .....                                    | 67  |
| FPGA Power Aspects and System Dependencies .....                   | 87  |
| Worst Case Power Analysis Using Xilinx Power Estimator (XPE) ..... | 98  |
| Configuration .....  | 102 |

### Chapter 4: Design Creation

|                                   |     |
|-----------------------------------|-----|
| Overview of Design Creation ..... | 104 |
|-----------------------------------|-----|

|   |     |
|---|-----|
| Defining a Good Design Hierarchy .....        | 105 |
| RTL Coding Guidelines .....                   | 108 |
| Clocking Guidelines .....                     | 157 |
| Working With Intellectual Property (IP) ..... | 204 |
| Working with Constraints .....                | 210 |

### Chapter 5: Implementation

|                                  |     |
|----------------------------------|-----|
| Overview of Implementation ..... | 255 |
| Synthesis .....                  | 255 |
| Synthesis Attributes .....       | 259 |
| Bottom Up Flow .....             | 261 |
| Moving Past Synthesis .....      | 263 |
| Implementing the Design .....    | 266 |
| Timing Closure .....             | 280 |
| Power .....                      | 327 |

### Chapter 6: Configuration and Debug

|   |     |
|---|-----|
| Overview of Configuration and Debug ..... | 338 |
| Configuration .....                       | 338 |
| Debugging .....                           | 344 |

### Appendix A: Baselining and Timing Constraints Validation Procedure


|                    |     |
|--------------------|-----|
| Introduction ..... | 358 |
|--------------------|-----|



## 4. Design flow and Performance, Power & Area (PPA) in FPGAs
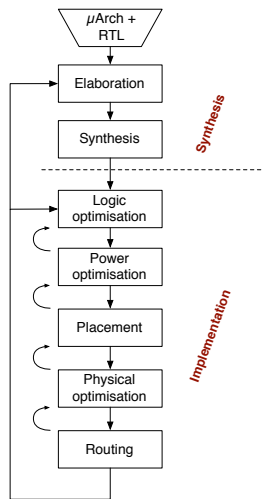
# Xilinx FPOGA design flow – optimization steps

- Actual flow adds extra steps on top of synthesis, place & route
- These aim **optimizations** to get best possible PPA; ICs are expensive, designs are complex and we & EDA tools should optimise PPA
- FPGA flow (Vivado) could be seen as push-button tool, and will work OK for small designs in one design iteration (if your design & constraints are OK)
- Real life (complex) designs may require **MANY iterations** at various stages
- Ultimate feedback is when you make a micro-architecture change; this is to be avoided since most time consuming



# I. Elaboration and Synthesis

- **Elaboration** – produces the logical view from the input RTL
  - ▷ Generated models are good for functional analysis and simulation, but doesn't (yet) involve **technology dependent mapping and optimization**
  - ▷ Analysis of elaborated design informs you on how good your RTL spec is against micro-architecture you have in mind
- **Synthesis** – provides technology dependent and somehow optimal (logical) view of your design; physical implementation properties are only estimated since the design is not routed yet:
  - a) **Area** – LUT/FF count and other resource usage
  - b) **Timing** – actual vs. supplied timing constraints
  - c) **Power** – statistically or simulation based
- If one of the above parameters doesn't meet the spec, there is no point of going further in the flow, since things will get worse with place & route!

## II. Logic & power optimization


- Post synthesis gate-level netlist is manipulated by the tool to further improve PPA during placement & routing
- Logic optimization methods include:
  - ▷ Logic trimming – suppression of unused, or not properly used logic
  - ▷ Logic remapping – further effort into logic-to-LUT translation that could possibly lead to even better overall LUT usage
  - ▷ RAM optimisations – FPGAs do contain dedicated memory instances, when do you use LUTs for memory and when the real memory instances?
- Power optimization – pre- or post- placement **but not both**;
  - ▷ Pre-placement power optimization transforms gate-level netlist and thus can affect timing for better or worse
  - ▷ Post-placement keeps the timing intact, but generally results in less power savings

### III. Placement

- Placement engine positions cells (LUTs) from the netlist onto specific sites in the target FPGA device ( $x,y$  locations)
- Placement constraints affect the placement engine
  - ▷ in a **good way** – they will provide hints where to look in the design space, and where not to spend efforts; improves PPA and run-time
  - ▷ in a **bad way** – bad constraints increase run-time with no visible effect, so this is waste of time & (electrical) energy (think of servers that run EDA SW)
- Quality constraints are crucial for a good design & are typically elaborated in iterative way: implement design (step-by-step), analyze PPA, modify constraints and re-run; constraints concern:
  - ▷ I/O or pin position
  - ▷ Location constraints for a given block (explicit physical constraints)
  - ▷ Timing Constraints – fundamental !!!
  - ▷ Netlist Constraints – ex. `LOCK_PINS`: used to specify mapping between logical LUT inputs and LUT physical input pins

 
# Physical optimization (1/2)

- Physical optimization is an **optional step** in the design flow
- It performs **timing-driven optimization** of all the paths that did not reach the timing
- Two methods: **retiming** and **logic replication**
  - ▷ **Retiming** – restructuring of FFs, i.e. changing the FF position to allow better timing on critical paths (better logic depth balance)
  - ▷ Latency remains unchanged since the same number of FFs
  - ▷ It is just the position of the FF in the critical path that changes (you could potentially do this yourself in RTL, but with effort)



 
# Physical optimization (2/2)

**Logic replication** – this is inverse to logic optimization, if applied it will increase area to gain performance



 If block C is in the critical path (other blocks are fixed) moving C to any other location will make things worse; if timing not met at this stage, we can't do anything



By replicating the block C we offer more flexibility for placement, contribution of wiring to critical path (logic will not be changed) can be reduced!

## IV. Routing

- All pins (terminals) in the design are connected using physical nets
  - ▷ Pins = all IO & intermediate logic, LUTs, memory, DSPs etc.
- Routing quality depends on target technology, design complexity (number of nets and pin) and constraints (timing or other)
- Routing is **timing driven**, optimization will aim to resolve all timing violations in the system
- **Poor routing results are often due to poor/incorrect timing constraints!**
- Routing can be fast, but unrealistic timing constraints could lead to uncontrolled run times, thus we usually limit the number of trials


| Design Route Status                |            |
|------------------------------------|------------|
|                                    | : # nets : |
| -----                              | -----      |
| # of logical nets.....             | 12400 :    |
| # of nets not needing routing..... | 4014 :     |
| # of internally routed nets.....   | 4014 :     |
| # of routable nets.....            | 8386 :     |
| # of fully routed nets.....        | 8386 :     |
| # of nets with routing errors..... | 0 :        |
| -----                              | -----      |

Routing report of a small design


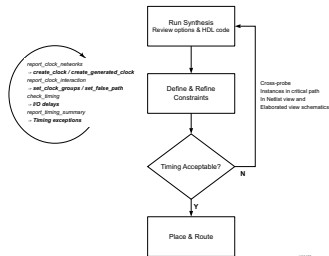
## V. Timing closure

- Process of completing the full place & route flow for a given HDL inputs, and EDA tools parameters that will produce a solution that **satisfies all constraints in the design**
- Constraints are typically refined as we move along with the flow and only when timing constraints are met at previous level, and with a certain margin, we can proceed with the next steps
- Good timing after synthesis will not guarantee good timing after routing
- In FPGA circuits **clock tree synthesis** (clock distribution to all FFs) & **power delivery** is fully automated and uses predefined resources; these two tasks could be quite complex in ASICs
- In FPGAs routing produces final design, extracted metrics are those of a circuit



# Constraints example

- Below we have **two clock periods** for two different clock nets
- Physical constraints for **FPGA pin positions**
  - ▷ These constraints are necessary to provide IC design that could be compatible with the existing PCB layout
  - ▷ If not specified, place & route tool does his own IO placement optimization (top-down, PCB to IC, or bottom-up, IC to PCB)
  - ▷ Placement of the LUTs will be driven by the IO placement

```
# LOC and IOSTANDARDS set for all IOs which is required for generating a Bitstream
create_clock -period 10 -name wbClk [get_ports wbClk]
create_clock -period 5 -name bftClk [get_ports bftClk]

# Since this sample design is not meant to be stand alone, but exist in a larger
# design, there are no input/output delays specified. Timing will not be done
# on these interfaces by default.
set_property PACKAGE_PIN P20 [get_ports {wbOutputData[23]}]
set_property PACKAGE_PIN V22 [get_ports {wbOutputData[9]}]
set_property PACKAGE_PIN E21 [get_ports {wbInputData[18]}]
set_property PACKAGE_PIN M17 [get_ports {wbInputData[4]}]
set_property PACKAGE_PIN R17 [get_ports {wbOutputData[22]}]
set_property PACKAGE_PIN T18 [get_ports {wbOutputData[8]}]
```

- Note that physical constraints are ignored during synthesis

## a) Area reporting 1/3

- **Total Logic Area ( $A_{TLA}$ )** – sum of the area of all logic resources in the design calculated after synthesis, placement & route
  - ▷ Logic resources = LUTs (and others) in FPGAs or gates in ASICs
- Ideally the total cell area should be equal to **total core (chip, IC) area  $A_{IC}$** , that is the actual silicon die area
- In practice this never happens, we always have some **unused area** due to place & route complexity
  - ▷ In ASICs this is some empty space in the IC, and in FPGAs this will be all unused LUTs (all those that are left non-programmed)
- Obviously unused area is to be minimized!
- To express how well silicon is used EDA tools use the notion of **Design Utilization** –  $DU$

$$DU = \frac{A_{TLA}}{A_{IC}}$$

## a) Area reporting 2/3

- Typically *DU* depends on the design complexity (mostly system connectivity), micro-architecture, designers skills, constraint realism, EDA tool chain ... and is probably the most important parameter designers are looking for since related to cost
- In ASICs *DU* can be from 75% and up to, but rarely, above 90%; in most recent CMOS nodes *DU* could be even less
- Sometimes designer accept exceptionally low *DU* (as low as 30%), but only for some parts of the design; certain functional blocks have complex connectivity and hence could result in complex place & route that needs space
- In FPGAs: you can pick the device density that suits the best the needs of the design, but don't expect utilization to be 100%
- Trying to get the high density will most likely degrade the system performance, since place&route have less freedom

## a) Area reporting 3/3

Example – post synthesis report provides: LUT usage (LUT implementing logic & memory!), flip-flops (latches) at **global** and **hierarchical** (per module) levels

### 1. Slice Logic

| Site Type             | Used | Fixed | Available | Util% |
|-----------------------|------|-------|-----------|-------|
| Slice LUTs*           | 4035 | 0     | 17600     | 22.92 |
| LUT as Logic          | 4035 | 0     | 17600     | 22.92 |
| LUT as Memory         | 0    | 0     | 6000      | 0.00  |
| Slice Registers       | 3098 | 0     | 35200     | 8.80  |
| Register as Flip Flop | 3098 | 0     | 35200     | 8.80  |
| Register as Latch     | 0    |       |           |       |
| F7 Muxes              | 0    |       |           |       |
| F8 Muxes              | 0    |       |           |       |

| Name                      | Slice LUTs*<br>(17600) | Slice Registers<br>(35200) | Block RAM Tile<br>(60) | DSPs<br>(80) | Bonded IOB<br>(100) | BUFGCTRL<br>(32) |
|---------------------------|------------------------|----------------------------|------------------------|--------------|---------------------|------------------|
| btr                       | 4036                   | 3098                       | 16                     | 64           | 71                  | 2                |
| arnd1 (round_1)           | 768                    | 384                        | 0                      | 16           | 0                   | 0                |
| arnd2 (round_2)           | 768                    | 384                        | 0                      | 16           | 0                   | 0                |
| arnd3 (round_3)           | 768                    | 384                        | 0                      | 16           | 0                   | 0                |
| arnd4 (round_4)           | 768                    | 384                        | 0                      | 16           | 0                   | 0                |
| egressLoop[0].egressFl... | 53                     | 94                         | 1                      | 0            | 0                   | 0                |
| egressLoop[1].egressFl... | 53                     | 94                         | 1                      | 0            | 0                   | 0                |
| egressLoop[2].egressFl... | 53                     | 94                         | 1                      | 0            | 0                   | 0                |
| egressLoop[3].egressFl... | 85                     | 94                         | 1                      | 0            | 0                   | 0                |
| egressLoop[4].egressFl... | 54                     | 94                         | 1                      | 0            | 0                   | 0                |
| egressLoop[5].egressFl... | 85                     | 94                         | 1                      | 0            | 0                   | 0                |
| egressLoop[6].egressFl... | 54                     | 94                         | 1                      | 0            | 0                   | 0                |
| egressLoop[7].egressFl... | 88                     | 94                         | 1                      | 0            | 0                   | 0                |
| ingressLoop[0].ingress... | 54                     | 94                         | 1                      | 0            | 0                   | 0                |
| ingressLoop[1].ingress... | 54                     | 94                         | 1                      | 0            | 0                   | 0                |
| ingressLoop[2].ingress... | 54                     | 94                         | 1                      | 0            | 0                   | 0                |
| ingressLoop[3].ingress... | 54                     | 94                         | 1                      | 0            | 0                   | 0                |
| ingressLoop[4].ingress... | 54                     | 94                         | 1                      | 0            | 0                   | 0                |

## b) Static Timing Analysis reports

- Gives us the following information:
  - ▷ **Worst Negative Slack (WNS)** – it is negative, the timing is not met for set-up! By adding 1.227ns to the target period you may end up with a right frequency target (you may re-run the full implementation flow with a new constraint)
  - ▷ **Total Negative Slack (TNS)** – 778.829ns; quite big compared to WNS
  - ▷ Finally the number of **failing endpoints** (number of failing paths); in the example below: 960 paths out of 7973 failed, roughly 10% this is a lot
  - ▷ Improving timing with HDL re-design could be hard; **constraints are too aggressive and should be relaxed**

| Design Timing Summary        |             |                              |          |  |          |
|------------------------------|-------------|------------------------------|----------|--|----------|
| Setup                        |             | Hold                         |          | Pulse Width                              |          |
| Worst Negative Slack (WNS):  | -1.227 ns   | Worst Hold Slack (WHS):      | 0.077 ns | Worst Pulse Width Slack (WPWS):          | 1.971 ns |
| Total Negative Slack (TNS):  | -778.829 ns | Total Hold Slack (THS):      | 0.000 ns | Total Pulse Width Negative Slack (TPWS): | 0.000 ns |
| Number of Failing Endpoints: | 960         | Number of Failing Endpoints: | 0        | Number of Failing Endpoints:             | 0        |
| Total Number of Endpoints:   | 7973        | Total Number of Endpoints:   | 7973     | Total Number of Endpoints:               | 3164     |

# Timing report at different implementation stages

- Below are shown two timing reports for the same design, first report is **post synthesis**, and the other is **post place & route**
- Design clearly did not meet timing specifications


| Design Timing Summary                                   |  |  |
|---|--|--|
| Setup   | Hold   | Pulse Width  |
| Worst Negative Slack (WNS): <a href="#">-1.227 ns</a>   | Worst Hold Slack (WHS): <a href="#">0.077 ns</a> | Worst Pulse Width Slack (WPWS): <a href="#">1.971 ns</a> |
| Total Negative Slack (TNS): <a href="#">-778.829 ns</a> | Total Hold Slack (THS): 0.000 ns                 | Total Pulse Width Negative Slack (TPWS): 0.000 ns        |
| Number of Failing Endpoints: <a href="#">960</a>        | Number of Failing Endpoints: 0                   | Number of Failing Endpoints: 0                           |
| Total Number of Endpoints: 7973                         | Total Number of Endpoints: 7973                  | Total Number of Endpoints: 3164                          |

| Design Timing Summary                                   |  |  |
|---|--|--|
| Setup   | Hold   | Pulse Width  |
| Worst Negative Slack (WNS): <a href="#">-1.400 ns</a>   | Worst Hold Slack (WHS): <a href="#">0.058 ns</a> | Worst Pulse Width Slack (WPWS): <a href="#">2.000 ns</a> |
| Total Negative Slack (TNS): <a href="#">-657.205 ns</a> | Total Hold Slack (THS): 0.000 ns                 | Total Pulse Width Negative Slack (TPWS): 0.000 ns        |
| Number of Failing Endpoints: <a href="#">940</a>        | Number of Failing Endpoints: 0                   | Number of Failing Endpoints: 0                           |
| Total Number of Endpoints: 7941                         | Total Number of Endpoints: 7941                  | Total Number of Endpoints: 3132                          |
| Timing constraints are not met.                         |  |  |

- There are slight differences; **Can you explain why?**
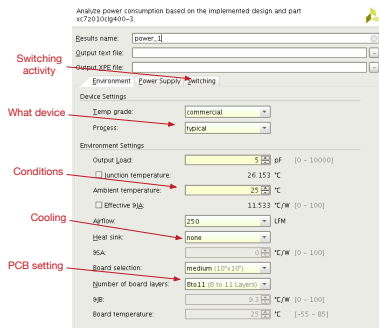
## c) Power reporting – setup


- Power simulation are run to derive electrical and thermal needs of the FPGA (power supply design and cooling)
- Assumptions are made on FPGA package, cooling and PCB; also we need logic activity; for quick power estimates **toggle statistics** are used, i.e. how much often gates/wires switch; common parameter for all gates – could under or over estimate
- **Accurate power simulation** – can be calculated only after routing & functional simulation that will provide exact switching activity of all gates & wires, i.e. which gate and wire switches and when; this is time consuming so done only at very end of the flow




 
## c) Power reporting – analysis

- Total power & temperature reported; note the **dynamic** (due to switching) and **static** (due to leakage) power components
- Detailed breakdown per IC component (Clock, wires, logic etc.)
  - ▷ What can you say about the breakdown?




- Note that the above report has been generated after synthesis, with no actual toggle statistics, hence the confidence is said to be low; this can be used as a rough guide

## 5. Physical implementation of FPGA circuits
 
# Implemented design

- Layout view of a placed circuit in an FPGA
- Current Vivado tool uses **analytical** placement & route engine to get more predictable results
- Nevertheless designers can use **randomness** when running the flow; this randomness could cause PPA differences (better or worse) of the implementation at the expense of longer run-times
- Using randomness could yield totally different layouts, although keeping exactly the same functionality
- Designers do not care how the design is implemented as long as:
  - ▷ it is a functionally correct,
  - ▷ that satisfies given timing & power constraints,
  - ▷ with minimum area since this will save cost



# FPGA configuration

- Once the timing is closed (i.e. constraints are validated), we can generate the corresponding **configuration file**, also known as a **bitstream**
  - ▷ **What exactly an FPGA configuration file stores?**
- Bitstream file contains design configuration information required to “program” a **given FPGA device** (you know why I use brackets)
  - ▷ When you start an FPGA project the first thing that you should do is to pick a certain FPGA device
  - ▷ FPGA manufactures group FPGAs in families, all devices in the same family share same architecture & CMOS node, but have **different capacity and speed grade**
  - ▷ FPGA device choice will influence design PPA & cost
- After the configuration file is loaded into FPGA device, design will run at specified (and supplied) frequency  $F$ ; FPGA devices do have their own internal clock generators, but you have limited choice

# Reconfigurable systems

- More & more computational systems are becoming **heterogeneous**: a combination of traditional general purpose CPUs and **HW accelerators** implemented using FPGAs
- Intel has bought Altera – 2nd FPGA manufacturer after Xilinx
  - ▷ **Why do you think they did so?**
- Some computing architectures use FPGAs to change their internal architecture depending on the computational problem they need to solve – **reconfigurable computer architecture**; new paradigm in computer architecture
- You have a library of configurations and you pick the one to be loaded in the FPGA circuit depending on the needs
- Of course you need to keep the interface of your reconfigurable architecture with everything else the same, but this is doable


# Dynamically reconfigurable systems

- Some FPGA devices allow **dynamic reprogrammability** – you define a part of the FPGA that could be modified on the fly, while the other part still remains operational – **dynamically reconfigurable computing**; a totally different view of computing systems compared to traditional programmable computing
- Connection between the configuration file source, typically some kind of re-programmable memory, & the FPGA itself is **serial** to limit configuration pin count (IC pins are expensive) and **not that fast** to allow use of longer cables
- Thus, the FPGA configuration takes **some non-negligible time** and this will limit how often the functionality is modified (these days you wouldn't do that that often)
- But tomorrow things may change ...
- **3D IC technologies** could be used to integrate very dense connections between FPGA and memory layers built on top
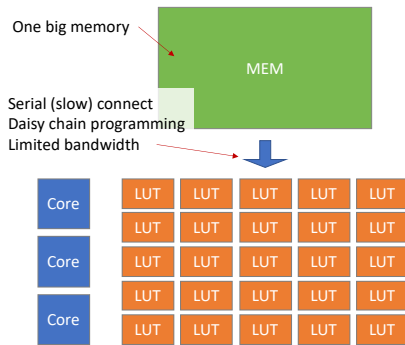
# 3D FPGA: is this the future?

By distributing the configuration memory and implementing it on-chip, reconfiguration time could be pushed to few memory cycles


Separate package with one configuration memory



In-package many configuration memories with


One or multiple layers of such memories

 3D-IC interconnect dense & fast high bandwidth


 
# Practical FPGA configurability

- Programming of the FPGA device can be done:
  - ▷ **Directly** – using your computer, FPGA IDE and some cable (JTAG is a commonly used standard) to directly program the device from the host computer
  - ▷ **Indirectly** – you store the bitstream into some kind of memory (e.g. flash); configuration stream is uploaded to the FPGA automatically during FPGA boot sequence on power-up
- When connected to a host computer and JTAG cable, designs can be tested **live** at run-time using **probes** to check values at certain points in the design
- Most of the FPGAs IDE provide some kind of support to recover probe values and display them for live debugging





# That's all folks!

