

# Lab04 – Hands on Experience with Basys3

## 1 7-Segment Display

### Top Module –

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_unsigned.all;

entity BCD_7SEG_TOP is Port (
CLK_100MHZ : in std_logic;
BCD_SW: in std_logic_vector (15 downto 0);
SEG_OUT: out std_logic_vector (6 downto 0);
ANODE_ACT: out std_logic_vector (3 downto 0)
); end BCD_7SEG_TOP;

architecture Behavioral of BCD_7SEG_TOP is
component Anode_Activate_SEG is Port (
CLK_100MHZ : in std_logic;
BCD_SW: in std_logic_vector (15 downto 0);
Anode_Activate: out std_logic_vector (3 downto 0);
SEG_BCD : out std_logic_vector (3 downto 0)
);end component;

component BCD_Deccoder is Port (
SEG_BCD : in std_logic_vector (3 downto 0);
SEG_OUT: out std_logic_vector (6 downto 0)
); end component;

signal BCD_CODE : std_logic_vector (3 downto 0);
begin
uul: Anode_Activate_SEG Port map( CLK_100MHZ => CLK_100MHZ, BCD_SW=>BCD_SW, SEG_BCD=>BCD_CODE
, Anode_Activate=>ANODE_ACT );
uu2: BCD_Deccoder Port map(SEG_BCD => BCD_CODE, SEG_OUT => SEG_OUT );
end Behavioral;

```

### SubModule – BCD Decoder

```

entity BCD_Deccoder is Port (
SEG_BCD : in std_logic_vector (3 downto 0);
SEG_OUT: out std_logic_vector (6 downto 0)
); end BCD_Deccoder;

architecture Behavioral of BCD_Deccoder is
begin
process (SEG_BCD)
begin
case SEG_BCD is
when "0000" => SEG_OUT <= "1000000"; -- "0"
when "0001" => SEG_OUT <= "1111001"; -- "1"
when "0010" => SEG_OUT <= "0100100"; -- "2"
when "0011" => SEG_OUT <= "0110000"; -- "3"
when "0100" => SEG_OUT <= "0011001"; -- "4"
when "0101" => SEG_OUT <= "0010010"; -- "5"
when "0110" => SEG_OUT <= "1000010"; -- "6"
when "0111" => SEG_OUT <= "1111000"; -- "7"
when "1000" => SEG_OUT <= "0000000"; -- "8"
when "1001" => SEG_OUT <= "0010000"; -- "9"
when "1010" => SEG_OUT <= "0100000"; -- a
when "1011" => SEG_OUT <= "0000011"; -- b
when "1100" => SEG_OUT <= "1000110"; -- c
when "1101" => SEG_OUT <= "1000010"; -- d
when "1110" => SEG_OUT <= "0000110"; -- e
when "1111" => SEG_OUT <= "0001110"; -- f
end case;
end process;
end Behavioral;

```

**Sub Module– Anode Activate SEG**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_unsigned.all;

entity Anode_Activate_SEG is Port (
CLK_100MHZ : in std_logic;
BCD_SW: in std_logic_vector (15 downto 0);
Anode_Activate: out std_logic_vector (3 downto 0);
SEG_BCD : out std_logic_vector (3 downto 0)
);
end Anode_Activate_SEG;

architecture Behavioral of Anode_Activate_SEG is
signal refresh_counter: std_logic_vector(19 downto 0);
signal SEG_active_Count: std_logic_vector(1 downto 0);

begin

process (CLK_100MHZ)
begin
    if(rising_edge(CLK_100MHZ)) then
        refresh_counter <= refresh_counter + 1;
    end if;
end process;
SEG_active_Count <= refresh_counter(19 downto 18);

process (SEG_active_Count)
begin
    case SEG_active_Count is
        when "00" => Anode_Activate <= "0111";
                        SEG_BCD <= BCD_SW(15 downto 12);
        when "01" => Anode_Activate <= "1011";
                        SEG_BCD <= BCD_SW(11 downto 8);
        when "10" => Anode_Activate <= "1101";
                        SEG_BCD <= BCD_SW(7 downto 4);
        when "11" => Anode_Activate <= "1110";
                        SEG_BCD <= BCD_SW(3 downto 0);
    end case;
end process;
end Behavioral;
```